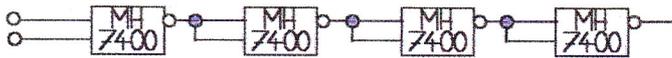


Cvičenie 22/3

Úloha cvičenia:


1. Navrhните 6 obvodov s hradlami IO MH7400 a MH7401.
2. Určite log stav na výstupe pri oboch možnostiach na vstupe.
3. Overtе zistený predpoklad na zapojení.

1.




A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

2.

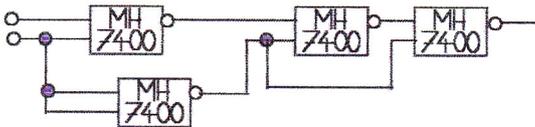

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	1


3.

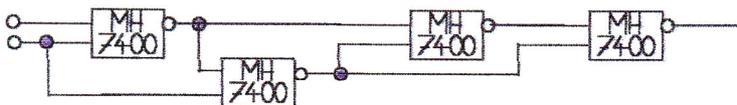

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0


Cvičenie 22/3

4.

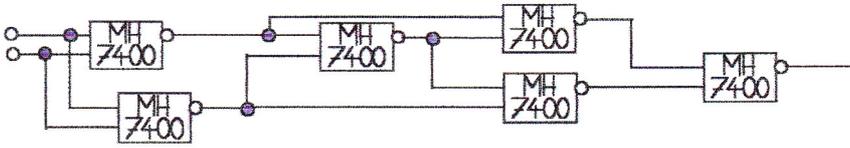


A	B	Y
0	0	0
0	1	0
1	0	0
1	1	0

5.

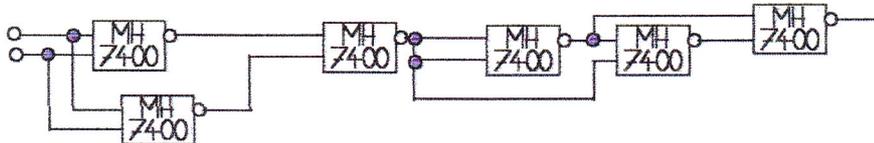

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

6.

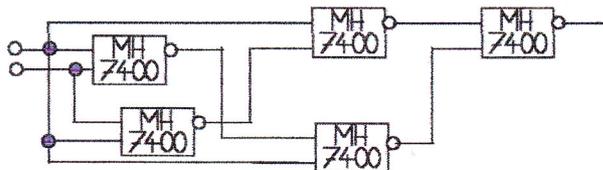

A	B	Y
0	0	0
0	1	0
1	0	1
1	1	0